



NAMAL UNIVERSITY, MIANWALI
Department of Electrical Engineering
EEN-214L- Electronic Devices & Circuits (Lab)
Project Report
“XOR gate using BJTs”

Name	Roll No.
Hassan Ali Ahmad	NUM-BSEE-2023-03
Raheem Bakhsh	NUM-BSEE-2023-10

Date:1/12/2025

Instructor: Zulakha Kiran
Lab Engineer: Engr. Muhammad Imtiaz-Ul-Hassan

Title project:**“XOR gate using BJT”****Abstract:**

The output of a BJT-based XOR gate depends on the state of inputs (A) and (B). The XOR logic dictates that output (Y) will be high (1) if only one input is high, while it will be low (0) if both inputs are equal e.g., when (A = 0) and (B = 0) is the value. 0) then no current flows through the circuit, resulting in (Y = 0). Similarly, if (A = 1) and (B = 1), the circuit is designed to connect the transistors in such a way that the output is disconnected, leaving (Y = 0). But if (A = 1) and (B = 0), or (A = 0) and (B = 1), a transistor drives a high output, (Y = 1). This switching behavior is validated by the careful configuration and biasing of the BJTs to the XOR logic truth table

Background:


An XOR (exclusive OR) table, the fundamental logic table, produces the higher sign (1) only when its two entries are different. When BJTs are used, the XOR table uses the switching properties of the transistors to achieve this understanding. By combining multiple BJTs with resistors and biasing mechanisms, the circuit ensures a desired output depending on the input condition. This application highlights how analog devices such as BJTs can perform digital logic functions, which is a foundational model in transistor-level circuit design.

Introduction:


This work demonstrates the implementation of an XOR logic gate using bipolar junction transistors (BJTs). The circuit uses several BJTs, resistors, and diodes to achieve XOR efficiency, with the output being high (argument 1) only when the two inputs are different the operation of the circuit can be summarized as follows.

1. **Case 1:** Input A = 0, B = 0 → Output = 0
2. **Case 2:** Input A = 0, B = 1 → Output = 1
3. **Case 3:** Input A = 1, B = 0 → Output = 1
4. **Case 4:** Input A = 1, B = 1 → Output = 0

Truth table:

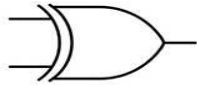	A	B	Output
	0	0	0
	1	0	1
	0	1	1
	1	1	0

Circuit diagram:

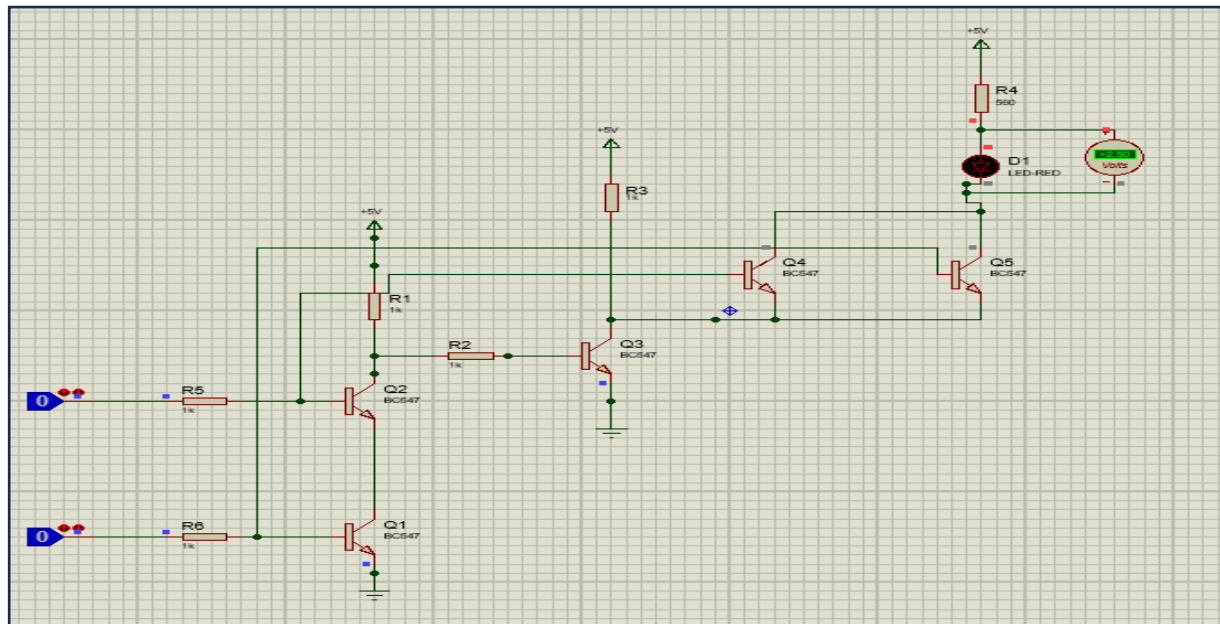

Equipment Required

Software

- Proteus

Hardware

- Five PN2222 Transistor
- Resistors
- Power supply
- Breadboard
- Connecting wires

Methodology

To solve the circuit first we have applied it on software to check the results and circuit.

Software implementation

By using above different components, circuit is built on proteus software.

All the components are taken from software library.


Procedure

After the software implementation we make the circuit on hardware setup. Then the results of input and output and written in report.

Simulation Results:

There are four possible case or XOR gate using BJT each case result description is given below:

Case=1 When both Switches are off

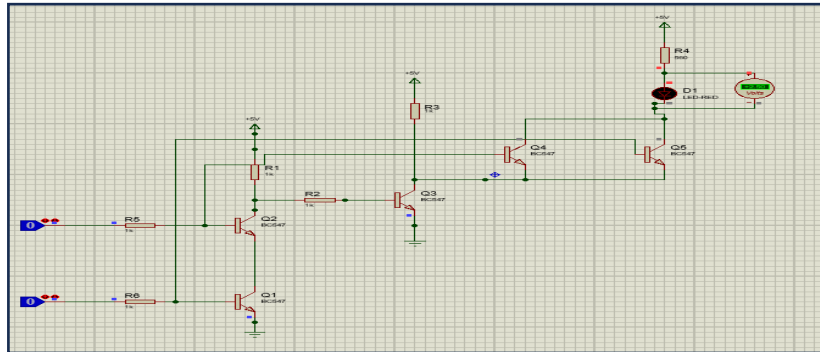

Circuit diagram


CASE=01 Results				
	Voltages		Currents	Regions
Transistor=01	VE=0	VBE=90.7mV	IE=3.2pA	Cut off region
	VB=90.7mV	VCE=78.57mV	IB=0.09pA	
	VC=78.6mV	VBC=12.12mV	IC=3.11pA	
Transistor=02	VE=78.8mV	VBE=88.69V	IE=3.25pA	Cut off region
	VB=167.3mV	VCE=3.22V	IB=3.18pA	
	VC=3.3V	VBC=3.13V	IC=0.07pA	
Transistor=03	VE=0	VBE=668.88mV	IE=12.67mA	Saturation region
	VB=668.9mV	VCE=34.25mV	IB=4.7mA	
	VC=34.4mV	VBC=634.63mV	IC=7.97mA	
Transistor=04	VE=34.25V	VBE=56.45mV	IE=1.08pA	Cut off region
	VB=90.7mV	VCE=7.97V	IB=0.09pA	
	VC=8V	VBC=7.91V	IC=0.99pA	
Transistor=05	VE=34.25mV	VBE=133mV	IE=17.3pA	Cut off region
	VB=167.3mV	VCE=7.97V	IB=0.07pA	
	VC=8V	VBC=7.83V	IC=17.22pA	

Description:

In the first case, when both buttons are off, the LED is off because this corresponds to the first case of the XOR gate truth table. When both inputs are low, the output is low. In this case, transistors one and two act as open circuits because there is zero voltage at their bases. Similarly, transistors four and five, which are connected to the bases of transistors one and two respectively, also act as open circuits due to zero voltage at their bases.

Since there is no complete path for the current from the battery connected to the LED, the LED remains off. In this case, transistors one, two, four, and five operate in the cutoff region

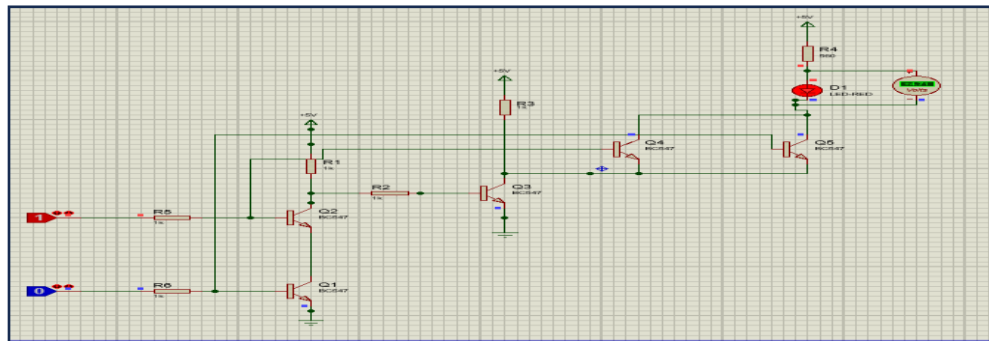Case=2
When 1st switch is on and 2nd switch is OFF




Circuit diagram:

CASE=02 Results				
	Voltages		Currents	Regions
Transistor=01	VE=0	VBE=664.4mV	IE=7.3mA	Saturation region
	VB=664.4mV	VCE=17.93mV	IB=7.3mA	
	VC=17.93mV	VBC=646.48mV	IC=14.11pA	
Transistor=02	VE=17.93mV	VBE=127.7mV	IE=14.11pA	Cut off region
	VB=145.7mV	VCE=7.29V	IB=0.04pA	
	VC=3.3V	VBC=3.16V	IC=14.07pA	
Transistor=03	VE=0	VBE=673.27mV	IE=15.88mA	Saturation region
	VB=673.3mV	VCE=38.83mV	IB=4.7mA	
	VC=38.83mV	VBC=634.4mV	IC=11.18mA	
Transistor=04	VE=38.83V	VBE=625.6mV	IE=3.19mA	Saturation region
	VB=664.4mV	VCE=6.03V	IB=31.9uA	
	VC=6.1V	VBC=5.41V	IC=3.19mA	
Transistor=05	VE=38.83V	VBE=106.36mV	IE=6.37pA	Cut off region
	VB=145.7mV	VCE=6.03V	IB=0.04pA	
	VC=6.1V	VBC=-5.93V	IC=6.33pA	

Description:

In the second case, when one button is on, the LED is on because this corresponds to the second case of the XOR gate truth table. When one input is high and the other is low, the output is high. In this case, there is voltage at the base of transistor one because the switch connected to its base is closed. Similarly, there is voltage at the base of transistor four because the bases of transistors one and four are connected to each other. Transistors two and five remain in an open-circuit state because the switches connected to their bases are also open. As a result, voltage reaches the base of transistor three because there is no alternate path for the current to follow. In this scenario, the current from the source connected to the LED completes its path, flowing from transistor four through transistor three to ground. The LED is on due to the complete path for current flow. In this case, transistors two and five operate in the cutoff region.

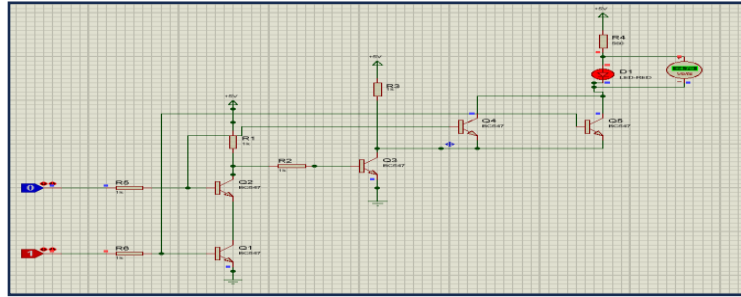Case=3
When 2nd Switch is on and 1st is OFF




Circuit diagram:

CASE=03 Results				
	Voltages		Currents	Regions
Transistor=01	VE=0	VBE=100.6mV	IE=5.04pA	Cut off region
	VB=100.6mV	VCE=635.56mV	IB=0.05pA	
	VC=635.6mV	VBC=500.97mV	IC=4.99pA	
Transistor=02	VE=635.6mV	VBE=100.86mV	IE=5.09pA	Cut off region
	VB=736.4mV	VCE=2.68V	IB=0.05pA	
	VC=3.3V	VBC=2.98V	IC=5.04pA	
Transistor=03	VE=0	VBE=688.92mV	IE=33.01mA	Saturation region
	VB=688.9mV	VCE=55.51mV	IB=4.70mA	
	VC=55.52mV	VBC=633.4mV	IC=28.31mA	
Transistor=04	VE=55.52mV	VBE=45.06mV	IE=0.43pA	Cut off region
	VB=100.6mV	VCE=35mV	IB=0.05pA	
	VC=90.55mV	VBC=10mV	IC=0.38pA	
Transistor=05	VE=55.52mV	VBE=681mV	IE=20.26mA	Saturation region
	VB=736.4mV	VCE=35.02mV	IB=7.26mA	
	VC=90.55mV	VBC=645.87V	IC=13.1mA	

Description:

In the third case, when the second button is on, the LED is on because this corresponds to the third case of the XOR gate truth table. When one input is high and the other is low, the output is high. In this case, there is voltage at the base of transistor two because the switch connected to its base is closed. Similarly, there is voltage at the base of transistor five because the bases of transistors one and five are connected to each other. Transistor one remains in a short-circuit state because the switch connected to its base is open. As a result, voltage reaches the base of transistor three because there is no alternate path for the current to follow. In this scenario, the current from the source connected to the LED completes its path, flowing from transistor five through transistor three to ground. The LED is on due to the complete path for current flow. In this case, transistors one and four operate in the cutoff region.

Case=4
When Both Switches are ON

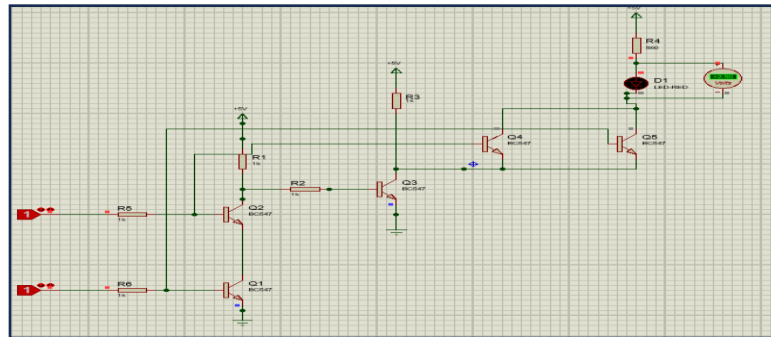

Circuit diagram

CASE=04 Results				
	Voltages		Currents	Regions
Transistor=01	VE=0V	VBE=682.9mV	IE=22.54A	Saturation region
	VB=682.9mV	VCE=36.91mV	IB=7.32mA	
	VC=36.91mV	VBC=645.98mV	IC=15.22mA	
Transistor=02	VE=36.91mV	VBE=675.6mV	IE=15.22mA	Saturation region
	VB=712.5mV	VCE=29.45mV	IB=7.29mA	
	VC=66.7mV	VBC=646.14mV	IC=7.93mA	
Transistor=03	VE=0V	VBE=66.37mV	IE=1.49pA	Cut off region
	VB=66.7mV	VCE=8V	IB=0.09pA	
	VC=8V	VBC=7.93V	IC=1.4pA	
Transistor=04	VE=8V	VBE=7.32V	IE=0.2pA	Saturation Region
	VB=682.9mV	VCE=0V	IB=0.1pA	
	VC=8V	VBC=7.2V	IC=0.1pA	
Transistor=05	VE=8V	VBE=7.29V	IE=0.2pA	Saturation Region
	VB=712.5mV	VCE=0V	IB=0.1pA	
	VC=8V	VBC=7.29V	IC=0.1pA	

Description:


In the fourth case, when both buttons are closed, the LED remains off. This corresponds to the fourth case of the XOR gate truth table, where both inputs are high, resulting in a low output. In this case, there is voltage at the base of transistors one and two because both switches connected to their bases are closed. Similarly, there is voltage at the bases of transistors four and five because their bases are connected to transistors one and two, respectively. However, no voltage reaches the base of transistor three because there is a shorter path for the current to flow through transistors one and two. As a result, the current from the source connected to the LED cannot complete its path because transistor three acts as an open circuit. The LED does not light up because there is no complete path for current flow. In this scenario, transistor three operates in the cutoff region.

Hardware:

There are also four possible cases for XOR gate using BJT each case result description is given below:

Case=1

When both the switches are OFF

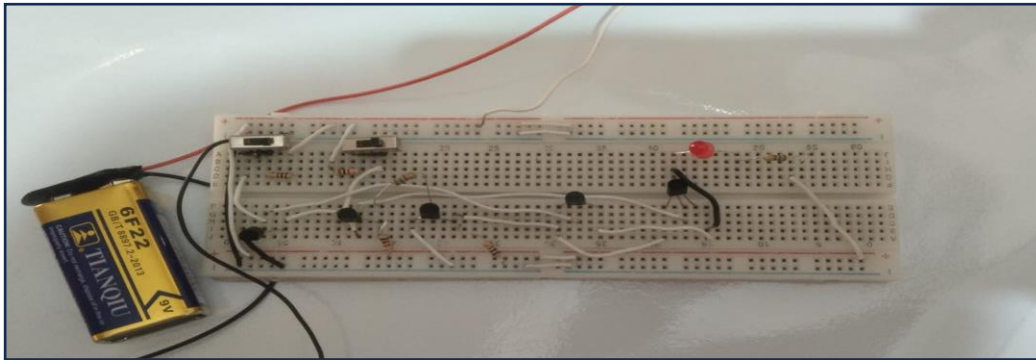

Circuit diagram:


CASE=01 Result				
	Voltages		Currents	Regions
Transistor=01	VE=0V	VBE=0.15V	IE=0A	Cut off region
	VB=0.25V	VCE=.002V	IB=0A	
	VC=0V	VBC=0.002V	IC=0A	
Transistor=02	VE=0.005V	VBE=0.129V	IE=0A	Cut off region
	VB=0.141V	VCE=0.004V	IB=0A	
	VC=3.414V	VBC=2.887V	IC=0A	
Transistor=03	VE=0V	VBE=0.775V	IE=12.4mA	Saturation region
	VB=0.776V	VCE=0.008V	IB=4.6mA	
	VC=0.01V	VBC=0.766V	IC=8mA	
Transistor=04	VE=0.01V	VBE=0.07V	IE=0A	Cut off region
	VB=0.054V	VCE=6.63V	IB=0A	
	VC=6.62V	VBC=6.03V	IC=0A	
Transistor=05	VE=0.01V	VBE=0.12V	IE=0A	Cut off region
	VB=0.16V	VCE=6.64V	IB=0A	
	VC=6.64V	VBC=5.8V	IC=0A	

Description:

In the first case, when both buttons are off, the LED is off because this corresponds to the first case of the XOR gate truth table. When both inputs are low, the output is low. In this case, transistors one and two act as open circuits because there is zero voltage at their bases. Similarly, transistors four and five, which are connected to the bases of transistors one and two respectively, also act as open circuits due to zero voltage at their bases.

Since there is no complete path for the current from the battery connected to the LED, the LED remains off. In this case, transistors one, two, four, and five operate in the cutoff region.

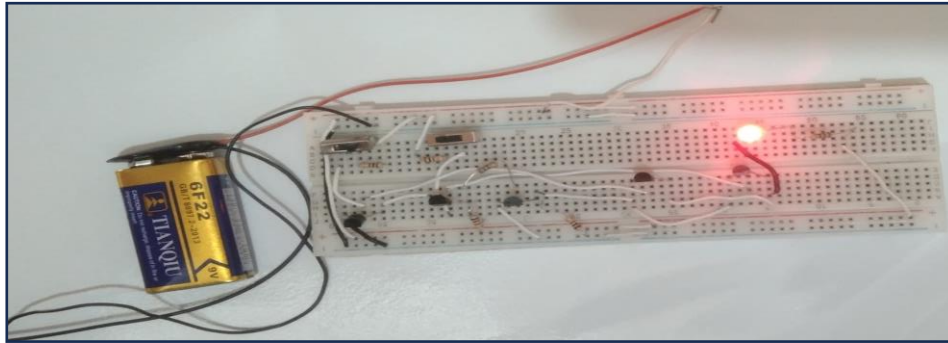Case=2
When 1st switch is on and 2nd switch is OFF




Circuit Diagram

CASE=02 Results				
	Voltages		Currents	Regions
Transistor=01	VE=0V	VBE=0.765V	IE=3.3 mA	Saturation region
	VB=.765V	VCE=0.002V	IB=3.3 mA	
	VC=0.002V	VBC=0.762V	IC=0 mA	
Transistor=02	VE=0.002V	VBE=0.261V	IE=0 mA	Cut off region
	VB=0.21V	VCE=3.41V	IB=0 mA	
	VC=3.417V	VBC=2.94V	IC=0 mA	
Transistor=03	VE=0V	VBE=0.782V	IE=13.6 mA	Saturation region
	VB=0.784V	VCE=0.017V	IB=4.6 mA	
	VC=0.019V	VBC=0.764V	IC=10.8 mA	
Transistor=04	VE=0.021V	VBE=0.74V	IE=7.5 mA	Saturation region
	VB=0.765V	VCE=0.15V	IB=1.3 mA	
	VC=0.065V	VBC=0.730V	IC=10.1 mA	
Transistor=05	VE=0.020V	VBE=0.09V	IE=0 mA	Cut off region
	VB=0.17V	VCE=0.01V	IB=0 mA	
	VC=0.32V	VBC=0.052V	IC=0 mA	

Description:

In the second case, when one button is on, the LED is on because this corresponds to the second case of the XOR gate truth table. When one input is high and the other is low, the output is high. In this case, there is voltage at the base of transistor one because the switch connected to its base is closed. Similarly, there is voltage at the base of transistor four because the bases of transistors one and four are connected to each other. Transistors two and five remain in an open-circuit state because the switches connected to their bases are also open. As a result, voltage reaches the base of transistor three because there is no alternate path for the current to follow. In this scenario, the current from the source connected to the LED completes its path, flowing from transistor four through transistor three to ground. The LED is on due to the complete path for current flow. In this case, transistors two and five operate in the cutoff region.

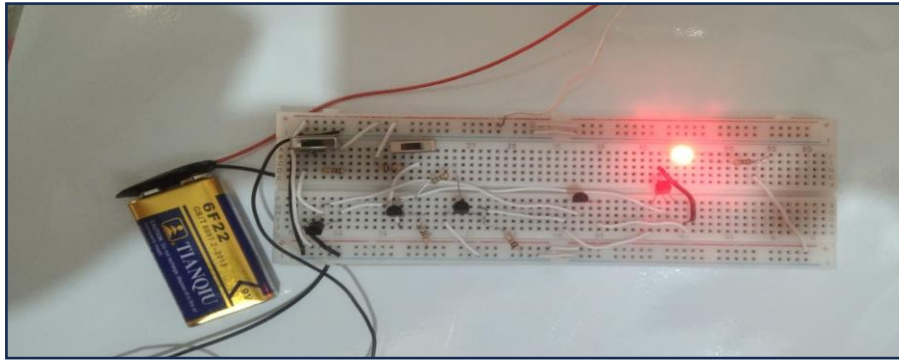Case=3
When 2nd Switch is on and 1st is OFF




Circuit Diagram

CASE=03 Result				
	Voltages		Currents	Regions
Transistor=01	VE=0V	VBE=0.21V	IE=0 mA	Cut off region
	VB=0.17V	VCE=0.58V	IB=0 mA	
	VC=0.64V	VBC=0.36V	IC=0 mA	
Transistor=02	VE=0.61V	VBE=0.1V	IE=0 mA	Cut off region
	VB=0.798V	VCE=0.001V	IB=0 mA	
	VC=4.17V	VBC=2.6V	IC=0 mA	
Transistor=03	VE=0V	VBE=0.784V	IE=29.1 mA	Saturation region
	VB=0.786V	VCE=0.21V	IB=4.6 mA	
	VC=0.024V	VBC=0.762V	IC=24.9 mA	
Transistor=04	VE=0.024V	VBE=0.1V	IE=0 mA	Cut off region
	VB=0.13V	VCE=0.01V	IB=0 mA	
	VC=0.036V	VBC=0.105V	IC=0 mA	
Transistor=05	VE=0.025V	VBE=0.77V	IE=17.1 mA	Saturation region
	VB=0.795V	VCE=0.01V	IB=7.1 mA	
	VC=0.035V	VBC=0.76V	IC=10.2 mA	

Description:

In the third case, when the second button is on, the LED is on because this corresponds to the third case of the XOR gate truth table. When one input is high and the other is low, the output is high. In this case, there is voltage at the base of transistor two because the switch connected to its base is closed. Similarly, there is voltage at the base of transistor five because the bases of transistors one and five are connected to each other. Transistor one remains in a short-circuit state because the switch connected to its base is open. As a result, voltage reaches the base of transistor three because there is no alternate path for the current to follow. In this scenario, the current from the source connected to the LED completes its path, flowing from transistor five through transistor three to ground. The LED is on due to the complete path for current flow. In this case, transistors one and four operate in the cutoff region.

Case=4
when both switches are ON

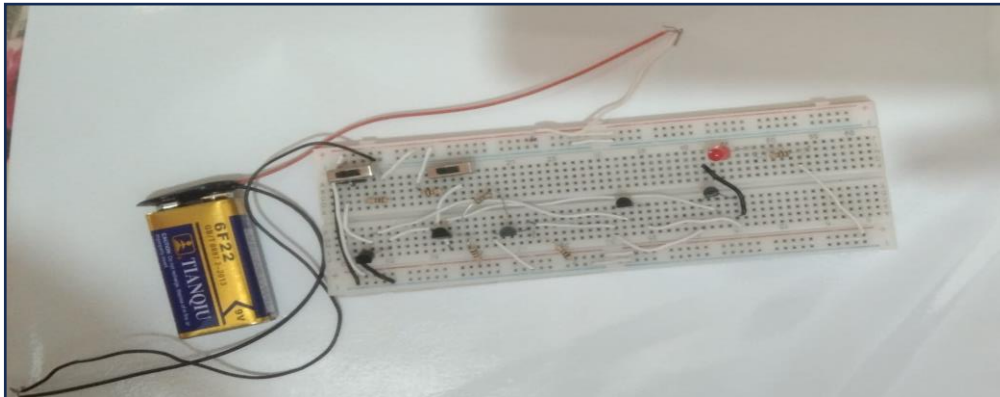

Circuit Diagram:

CASE=04 Results				
	Voltages		Currents	Regions
Transistor=01	VE=0V	VBE=0.78V	IE=2.2 mA	Saturation region
	VB=781V	VCE=0.011V	IB=7.1 mA	
	VC=0.01V	VBC=0.769V	IC=15.2 mA	
Transistor=02	VE=0.12V	VBE=0.768V	IE=15.1 mA	Saturation region
	VB=0.78V	VCE=0.08V	IB=7.2 mA	
	VC=0.021V	VBC=0.759V	IC=4.8 mA	
Transistor=03	VE=0V	VBE=0.021V	IE=0 mA	Cut off region
	VB=0.021V	VCE=8.09V	IB=0 mA	
	VC=8.07V	VBC=8.04V	IC=0 mA	
Transistor=04	VE=8.07V	VBE=7.29V	IE=0 mA	Saturation Region
	VB=0.77V	VCE=0V	IB=0 mA	
	VC=6.61V	VBC=5.87V	IC=0 mA	
Transistor=05	VE=8.05V	VBE=7.3V	IE=0 mA	Saturation Region
	VB=0.77V	VCE=0V	IB=0 mA	
	VC=6.62V	VBC=5.89V	IC=0 mA	

Description:

In the fourth case, when both buttons are closed, the LED remains off. This corresponds to the fourth case of the XOR gate truth table, where both inputs are high, resulting in a low output. In this case, there is voltage at the base of transistors one and two because both switches connected to their bases are closed. Similarly, there is voltage at the bases of transistors four and five because their bases are connected to transistors one and two, respectively. However, no voltage reaches the base of transistor three because there is a shorter path for the current to flow through transistors one and two. As a result, the current from the source connected to the LED cannot complete its path because transistor three acts as an open circuit. The LED does not light up because there is no complete path for current flow. In this scenario, transistor three operates in the cutoff region.

Application [4]

- **Arithmetic operations:** XOR gates are used in half-adders and full-adders to calculate the sum and carry of two- or three-bit numbers.
- **Parity checking:** XOR gates can determine if a binary number has an odd or even number of 1's. This is called the parity bit, and it can be used to check for errors in transmitted data.
- **Cryptography:** XOR logic can be used as a simple cipher to encrypt and decrypt messages.
- **Pseudo-random number generation:** A suitable XOR gate can be used to generate pseudo-random numbers.
- **Programmable inverter:** XOR gates can function as an inverter that can be activated or deactivated by a switch.
- **Comparators:** XOR gates are used in comparators.
- **Subtractors:** XOR gates are used in subtractors.
- **Boolean equations:** XOR gates can be used to simplify Boolean equations.

DISCUSSION OF RESULTS

All possible input combinations of the XOR table using BJTs were tested, and the results were checked to confirm the XOR logic. The circuit exhibited the expected behavior as follows.

Case 1: Inputs A = 0, B = 0 → Output = 0 (LED off):

When both inputs were set to 0, no current flowed through the output stage, as expected. The LED remained off, representing the lowest output (logic 0).

Case 2: Input A = 0, B = 1 → Output = 1 (LED on):

With this input combination, the circuit activated only one transistor, allowing current to flow in the output stage. The LED turned on, indicating a high output (logic 1). This XOR corresponds to the truth table.

Case 3: Inputs A = 1, B = 0 → Output = 1 (LED on):

Similar results were obtained with this design, providing a transistor, allowing current to flow in the output stage. The LED flashes, confirmed as high (logic 1).

Case 4: Inputs A = 1, B = 1 → Output = 0 (LED off):

In this case, both transistors were used simultaneously, leaving the output stage intact due to the design of the circuit. The LED remained off, confirming a low output (logic 0).

These results are in good agreement with the XOR truth table, where the results increase only when the inputs are different. The circuit demonstrated the ability to reliably implement XOR logic through BJTs. The use of LEDs for output visualization made it easier to verify the logic in real time. This successful application highlights the efficient use of BJTs in digital logic circuits and.

Conclusion:

In conclusion, we constructed an XOR gate using five transistors, which efficiently fulfills the XOR gate truth table. In the simulation, we provided an input of five volts, and in the hardware implementation, we used eight volts. We implemented the design in both cases hardware and software and observed the results of current flow and the region of operation of the transistors under different conditions. The output efficiently matched the XOR gate truth table.

REFERENCES:

1. <https://www.youtube.com/watch?v=sTu3LwpF6XI&t=660s&pp=ygUlaG93IHRvIG1ha2UgeG9yIGdhGUGdXNpbmcgdHJhbnNpc3Rvcg%3D%3D>
2. <https://www.gsnetwork.com/xor-gate/>
3. <https://circuitdigest.com/electronic-circuits/how-to-build-xor-logic-gate-using-transistors>
4. https://www.google.com/search?q=APPLICATION+OF+XORGATE+BY+TRANSISTOR&sca_esv=ad1fa8e7d3282536&sxsrf=ADLYWIIJq2fjXV0p2tzlyPLnEmxLIVsXqgg%3A1736598836212&ei=NGWCZ4PDLOC9u8PvYjBwQE&ved=0ahUKEwiPuf_l1u2KAXUzgf0HHT1EMBgQ4dUDCBA&uact=5&oq=APPLICATION+OF+XORGATE+BY+TRANSISTOR&gs_l=Egxnd3Mtd2l6LXNlcnAiJEfQUExJQ0FUSU90IE9GIFhPUkdBVEUgQlkgVFJBTINJU1RPUjIHECEYoAEYCKjHelCVAIjgdXACeAGQAQCYAegCoAHfIKoBBjltMTluM7gBA8gBAPgBAZgCEaACxyHCAgoQABiwAxjWBBhHwgINEAAYgAQYsAMYQxiKBclCBxAAGIAEGA3CAgYQABgWGB7CAGgQABgFGA0YHsICCBAAGAgYDRgewglLEAAYgAQYhgMYigXCAGgQABiABBiiBMICBBAhGBXCAGQQIRgKwglFECEYnwWYAwDiAwUSATegQlgGAZAGCpIHCDluMC4xMi4zoAe3Sw&sclient=gws-wiz-serp